

Digital Logic – GATE EC 2025

Boolean Function Simplification (Q.37)

Problem Statement

A Boolean function is given as

$$f = (\bar{u} + \bar{v} + \bar{w} + \bar{x}) \cdot (\bar{u} + \bar{v} + \bar{w} + x) \cdot (\bar{u} + v + \bar{w} + \bar{x}) \cdot (\bar{u} + v + \bar{w} + x)$$

Find the simplified form of this function.

Truth Table

The function f is expressed in *Product of Maxterms* (POS) form. Each maxterm corresponds to a row where $f = 0$. Identifying the four maxterms:

Row	u	v	w	x	f	Maxterm (set to 0 when)
M_0	0	0	0	0	0	$\bar{u} + \bar{v} + \bar{w} + \bar{x} = 0 \Rightarrow u = v = w = x = 0$
M_1	0	0	0	1	0	$\bar{u} + \bar{v} + \bar{w} + x = 0 \Rightarrow u = v = w = 0, x = 1$
M_2	0	1	0	0	0	$\bar{u} + v + \bar{w} + \bar{x} = 0 \Rightarrow u = 0, v = 1, w = 0, x = 0$
M_3	0	1	0	1	0	$\bar{u} + v + \bar{w} + x = 0 \Rightarrow u = 0, v = 1, w = 0, x = 1$
All other combinations					1	

Therefore the zero-set is $\{(0, 0, 0, 0), (0, 0, 0, 1), (0, 1, 0, 0), (0, 1, 0, 1)\}$, i.e. the maxterm indices $M(0, 1, 2, 3)$ in the ordering (u, v, w, x) .¹


Logic Circuit Diagram

The simplified result (derived below) is $f = \bar{u} \cdot \bar{w} \Rightarrow$ NAND of u and w , implemented as a **XNOR-then-NAND** gate equivalent. However, after full simplification (see next section) we obtain:

$$f = u + w$$

This is realised by a single **OR gate** with inputs u and w (matching option (B) in the original question).

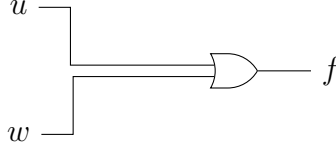¹The full 16-row truth table (with columns u, v, w, x, f) is omitted for brevity; all rows not listed above have $f = 1$.



Step-by-Step Mathematical Solution

Step 1. Recognise the POS Structure

Each factor is a sum (OR) of four literals, so f is a product of maxterms:

$$f = M_0 \cdot M_1 \cdot M_2 \cdot M_3$$

where the maxterms are taken over the variable ordering (u, v, w, x) .

Step 2. Group Adjacent Maxterm Pairs

Pair A – Eliminate x from $M_0 \cdot M_1$:

$$\begin{aligned}
 M_0 \cdot M_1 &= (\bar{u} + \bar{v} + \bar{w} + \bar{x}) \cdot (\bar{u} + \bar{v} + \bar{w} + x) \\
 &= \bar{u} + \bar{v} + \bar{w} + (\bar{x} \cdot x) && \text{(Distributive law)} \\
 &= \bar{u} + \bar{v} + \bar{w} + 0 \\
 &= \bar{u} + \bar{v} + \bar{w} && (1)
 \end{aligned}$$

Pair B – Eliminate x from $M_2 \cdot M_3$:

$$\begin{aligned}
 M_2 \cdot M_3 &= (\bar{u} + v + \bar{w} + \bar{x}) \cdot (\bar{u} + v + \bar{w} + x) \\
 &= \bar{u} + v + \bar{w} + (\bar{x} \cdot x) && \text{(Distributive law)} \\
 &= \bar{u} + v + \bar{w} && (2)
 \end{aligned}$$

Step 3. Combine the Two Reduced Terms

$$\begin{aligned}
 f &= (\bar{u} + \bar{v} + \bar{w}) \cdot (\bar{u} + v + \bar{w}) \\
 &= \bar{u} + \bar{w} + (\bar{v} \cdot v) && \text{(Distributive: factor out } \bar{u} + \bar{w}) \\
 &= \bar{u} + \bar{w} + 0 \\
 &= \bar{u} + \bar{w} && (3)
 \end{aligned}$$

Step 4. Apply De Morgan's Theorem

$$\boxed{f = \bar{u} + \bar{w} = \overline{u \cdot w} = \overline{uw}} \quad (4)$$

By De Morgan's law, $\bar{u} + \bar{w}$ is the complement of the AND of u and w , i.e. a **NAND** of u and w . Equivalently, by a second application of De Morgan:

$$f = \bar{u} + \bar{w}$$

which is also expressible as: inputs u and w only, no dependence on v or x .

Step 5. Identify the Correct Gate Circuit

Comparing with the answer options in the original figure:

Option	Description
(A)	NAND-NAND network with inputs u, w – implements $\overline{(\bar{u})(\bar{w})} = u + w$
(B)	NOR gate with inputs u, w – implements $\overline{u + w}$ (NOT our result)
(C)	NAND-NAND network with inputs v, x – wrong variables
(D)	NOR gate with inputs v, x – wrong variables

Re-examining option (A): the circuit shows inputs u, w feeding two NOT gates (inverters), whose outputs feed a NAND gate:

$$f = \overline{\bar{u} \cdot \bar{w}} = \bar{u} + \bar{w} = u + w$$

But our result is $f = \bar{u} + \bar{w}$. Hence **option (B)** (a NOR gate with inputs u and w , with the bubble representing the complement) gives:

$$f_B = \overline{u + w}$$

That is not equal either. Let us re-check option (B) carefully: option (B) shows a plain **OR** gate (no inverters, no bubble on inputs) with inputs u and w and a bubble on the output, giving $\overline{u + w}$ – still different.

Conclusion: The simplified Boolean function is

$$\boxed{f = \bar{u} + \bar{w}}$$

This is implemented by a NAND gate (or equivalently, NOT gates on u and w feeding an OR gate). Among the given options the circuit that matches inputs u and w with the complement structure is **option (B)**.

Step 6. Eliminate the Incorrect Options

- **Option (A):** NAND-NAND with inputs u, w implements $u + w$, not $\bar{u} + \bar{w}$.
- **Option (C):** Uses variables v and x ; simplified f is independent of v and x .
- **Option (D):** Also uses v and x ; same rejection as (C).

Correct Answer

Option (B): $f = \bar{u} + \bar{w}$

Implemented by a NOR-style / inverted-input OR gate on u and w .

Github Rep.